

Figure 1 - the microcontroller module has important critical parts that need to be identified before the PCB design

2. Similarly, analyze the USB module (Figure 2):

- Which part prevents noise to propagate over the bus power supply?
- How does the electrostatic discharge (ESD) protection circuit work?
- The ESD pulses are fast changing signals. How should the return path for the ESD pulse be designed – in terms of the return path impedance?
- What is the role of the series resistors R40 and R41?
- Where should you place the components that are the first components that USB signals reach coming from the USB connector?
- The USB communication is based on a fast differential signal pair. How should this fast differential signals be routed on the PCB in order to minimize the EMI?

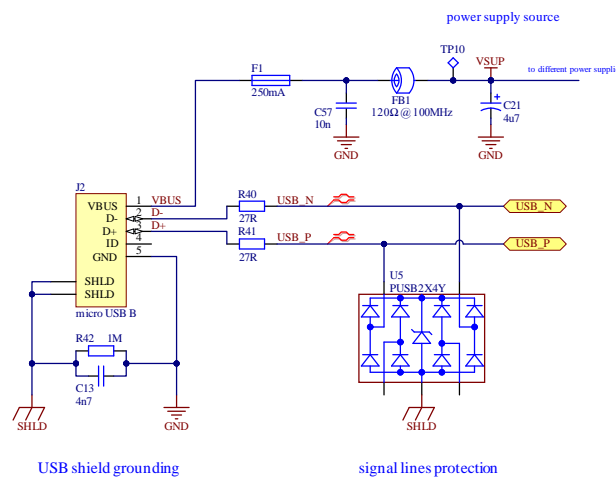


Figure 2 - you will design the USB part

3. Design the microcontroller module and the USB module.

Advice: make sure that the microcontroller location and orientation are suitable (consider the location of other modules). Then, make a good detailed placement of components. Start with the most critical components and proceed to the less critical components. When you are happy with the component placement, start routing the connections. Again, from the most critical to the less critical. Do not forget to place the ground vias. Try to minimize the segmentation of the ground polygon pour beneath the microprocessor. Use the idea of "fanout routing" to achieve this (see additional materials).

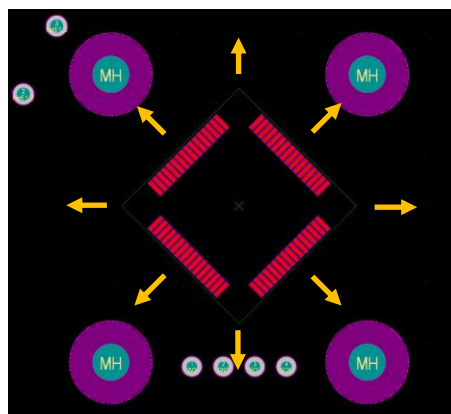


Figure 3 - deciding where exactly to place the microcontroller so that you will have enough room for all the important components that should be near the microcontroller. The issue here are the obstacles surrounding the microcontroller (i.e. the holes and locked component pins).

Explanation of the exercise

We are moving the focus of our PCB design to the center of the PCB, where you will design the microcontroller part. Microcontrollers are, of course, widely used in electronics: from very simple devices to complex systems. Therefore it is important that you are aware of the potential problems that come with the microcontroller PCB design and that you know how to deal with them.

Preparation for the lab exercise

You can refresh the knowledge about [the bypass capacitors and their appropriate application](#).

Also, you can refresh the knowledge about [the fast signals and their ground return paths](#).